

Домашняя работа №3

Задача №1


1.1. Дано:

$$U_{LED} = 3,2 \text{ В}$$

$$I_{LED} = I_L = 20 \text{ мА}$$

$$U_{CC} = 7,4 \text{ В}$$

$$R_{E24} = ? \quad P = ?$$

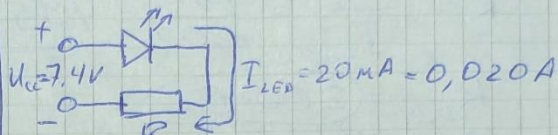

$$U_R = U_{CC} - U_{LED} = 7,4 - 3,2 = 4,2 \text{ В}$$

$$R = \frac{U_R}{I_{LED}} = \frac{4,2}{0,02} = 210 \text{ Ом}$$

$$R_{E24} = 220 \text{ Ом}$$

$$P = \frac{U^2}{R_{E24}} = 0,08 \text{ Вт} = 80 \text{ мВт} \rightarrow P_{0603} = 0,1 \text{ Вт}$$

Ответ: $R_{E24} = 220 \text{ Ом}$; $P_{0603} = 0,1 \text{ Вт}$.

1.2 Дано:

$$U_{CC} = 11,7 \text{ В}$$

$$I_{LED} = 20 \text{ мА}$$

$$U_{LED} = 2,25 \text{ В}$$

$$n_{LED} = 2 \text{ шт.}$$

$$R_{E24} = ? \quad P = ?$$



$$U_R = U_{CC} - n_{LED} \cdot U_{LED} = 11,7 - 2 \cdot 2,25 = 7,2 \text{ В}$$

$$R = \frac{U_R}{I_{LED}} = \frac{7,2}{0,02} = 360 \text{ Ом}$$

$$R_{E24} = 360 \text{ Ом}$$

$$P = \frac{U^2}{R_{E24}} = 0,144 \text{ Вт}; \quad P_{1206} = 0,25 \text{ Вт}$$

Ответ: $R_{E24} = 360 \text{ Ом}$; $P_{1206} = 0,25 \text{ Вт}$.

1.3 Дано:

$$U_{CC} = 12,7 \text{ В}$$

$$I_{LED} = 20 \text{ мА}$$

$$U_{LED} = 2,2 \text{ В}$$

$$n_{LED} = 16 \text{ шт.}$$

$$n_{расч.} = ?; R = ?; P_R = ?$$

$$U_{LED \times 16} = 16 \cdot U_{LED} = 16 \cdot 2,2 \text{ В} = 35,2 \text{ В} \quad \times$$

$$U_{LED \times 8} = 8 \cdot U_{LED} = 8 \cdot 2,2 = 17,6 \text{ В} \quad \times$$

$$U_{LED \times 4} = 4 \cdot U_{LED} = 4 \cdot 2,2 = 8,8 \text{ В} \Rightarrow N = 4 \text{ шт.}$$



$$U_R = 12,7 - 8,8 = 3,9 \text{ В}$$

$$R = \frac{U_R}{I_{LED}} = \frac{3,9}{0,02} = 195 \text{ Ом}$$

$$R_{E24} = 200 \text{ Ом}$$

$$P_R = \frac{U^2}{R} = \frac{3,9^2}{200} = 0,076 \text{ Вт}$$

$$P_{0603} = 0,1 \text{ Вт}$$

Ответ: $R_{E24} = 200 \text{ Ом}$; $P_{0603} = 0,1 \text{ Вт}$

Задача №2


2.1 Дано:

$$U_{CC} = 12,7 \text{ В}$$

$$U_2 = 8,4 \text{ В}$$

$$R_1 = 220 \text{ Ом}$$

$$R_2 = ?$$

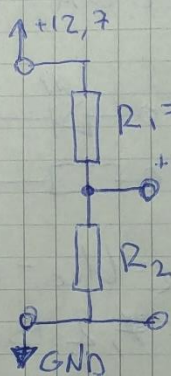

$$\frac{R_1}{R_2} = \frac{U_1}{U_2'}$$

$$R_2 = \frac{R_1 \cdot U_2}{U_1}$$

$$U_1 = U_{CC} - U_2 = 12,7 - 8,4 = 4,3 \text{ В}$$

$$R_2 = \frac{220 \cdot 8,4}{4,3} = 430 \text{ Ом}; \quad I = \frac{U_{CC}}{R_1 + R_2} = \frac{12,7}{220 + 430} = 0,02 \text{ А}$$

Ответ: $R_2 = 430 \text{ Ом}$


2.2 Дано:

$$U_{CC} = 6,8 \text{ В}$$

$$U_2 = 3,4 \text{ В}$$

$$R_1 = 82 \text{ Ом}$$

$$R_2 = ?$$

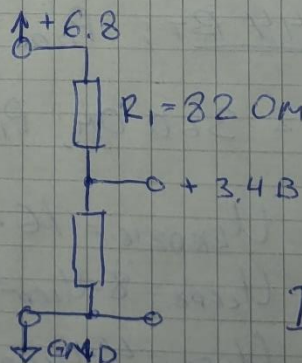

$$U_2 = \frac{U_{CC}}{2}$$

⇓

$$R_1 = R_2$$

$$R_2 = 82 \text{ Ом}$$

$$I = \frac{U_{CC}}{R_1 + R_2} = \frac{6,8}{82 + 82} = 0,04 \text{ А}$$

Ответ: $R_2 = 82 \text{ Ом}$

2.3.1 Дано:

$$U_{cc} = 12,7 \text{ В}$$

$$U_2 = 8,4 \text{ В}$$

$$R_1 = 2200 \text{ Ом}$$

$$I_{\text{нагр}} = 0,007 \text{ А}$$

$$R_2 = ?$$

$$R_{\text{нагр}} = \frac{U_2}{I_{\text{нагр}}} = \frac{8,4}{0,007} = 12000 \text{ Ом}$$

$$R_{2\varepsilon} = 4300 \text{ Ом (ср. 2.1)}$$

$$R_{2\varepsilon} = \frac{R_2 \cdot R_{\text{нагр}}}{R_2 + R_{\text{нагр}}}$$

$$R_{2\varepsilon} \cdot R_2 + R_{2\varepsilon} \cdot R_{\text{нагр}} - R_2 \cdot R_{\text{нагр}} = 0$$

$$R_2 = \frac{R_{2\varepsilon} \cdot R_{\text{нагр}}}{R_{\text{нагр}} - R_{2\varepsilon}} = \frac{430 \cdot 1200}{1200 - 430} =$$

$$= 670,13 \text{ Ом}$$

$$\text{Ответ: } R_2 \approx 670 \text{ Ом}$$

2.3.2 Дано:

$$U_{cc} = 6,8 \text{ В}$$

$$U_2 = 3,4 \text{ В}$$

$$R_1 = 820 \text{ Ом}$$

$$I_{\text{нагр}} = 0,007 \text{ А}$$

$$R_2 = ?$$

$$R_{\text{нагр}} = \frac{U_2}{I_{\text{нагр}}} = \frac{3,4}{0,007} = 485,7 \text{ Ом}$$

$$R_{2\varepsilon} = 820 \text{ Ом (2.2)}$$

$$R_{2\varepsilon} = \frac{R_2 \cdot R_{\text{нагр}}}{R_2 + R_{\text{нагр}}}$$

$$R_2 = \frac{R_{2\varepsilon} \cdot R_{\text{нагр}}}{R_{\text{нагр}} - R_{2\varepsilon}} = \frac{82 \cdot 485,7}{485,7 - 82} =$$

$$= 98,66 \text{ Ом}$$

$$\text{Ответ: } R_2 \approx 100 \text{ Ом}$$

Задача N3

$$t_{95} = 3 \cdot \tau = 3 \cdot R \cdot C$$

$$3.1 \quad R = 820 \text{ Ом}; C = 2,2 \text{ мкФ} = 2,2 \cdot 10^{-6} \text{ Ф}$$

$$t_{95} = 3 \cdot 2,2 \cdot 82 \cdot 10^{-6} = 541,2 \cdot 10^{-6} \text{ с} \approx 0,54 \text{ мс}$$


$$3.2 \quad R = 6,8 \text{ Ом}; C = 33 \text{ мкФ} = 33 \cdot 10^{-6} \text{ Ф}$$

$$t_{95} = 3 \cdot 6,8 \cdot 33 \cdot 10^{-6} = 673,2 \cdot 10^{-6} \text{ с} \approx 0,67 \text{ мс}$$

$$3.3 \quad R = 1,8 \text{ кОм} = 1800 \text{ Ом}; C = 0,47 \text{ нФ} = 0,47 \cdot 10^{-9} \text{ Ф}$$

$$t_{95} = 3 \cdot 1800 \cdot 0,47 \cdot 10^{-9} = 2538 \cdot 10^{-9} \text{ с} \approx 2,5 \text{ мкс}$$

Task #1

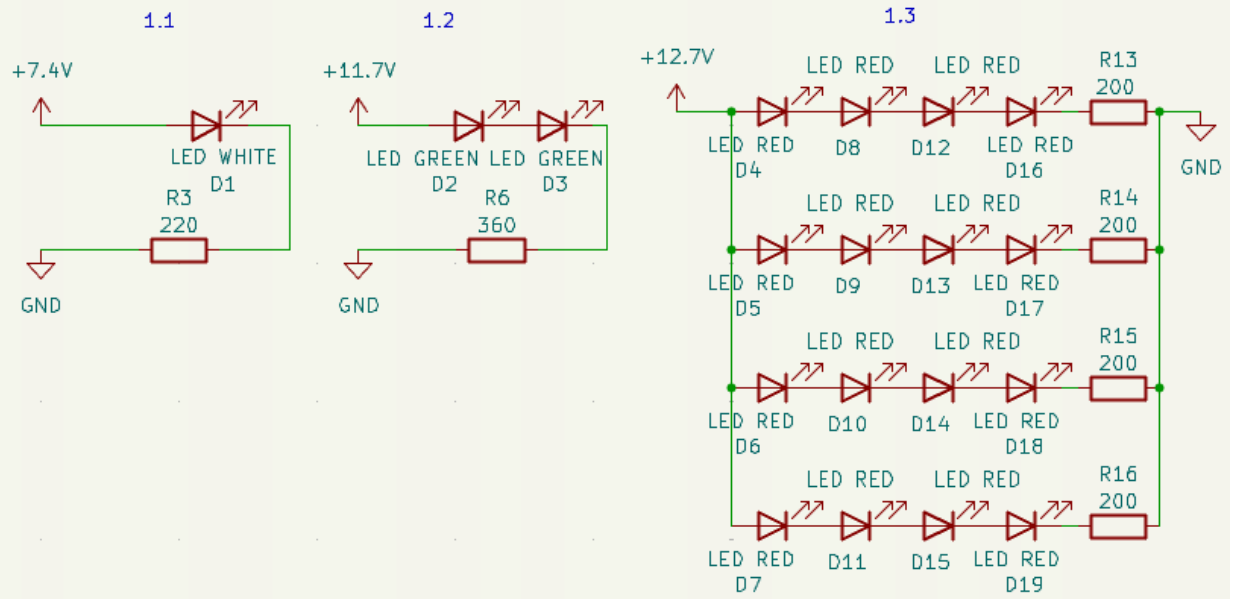

Task #2

